

# ECEn/CS 224

## Chapter 14 Homework Solutions

- 14.1 Design a 2-bit gray code counter with a CLR input and a INC input. In the case CLR = INC = '1', have the counter also increment.


CLR	INC	Q <sub>1</sub>	Q <sub>0</sub>	N <sub>1</sub>	N <sub>0</sub>
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	1	0

		CLR INC			
Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
N <sub>1</sub>	00				
	01		1	1	
	11	1	1	1	
	10	1			

		CLR INC			
Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
N <sub>0</sub>	00		1	1	
	01	1	1	1	
	11	1			
	10				

$$N_1 = \text{INC} \cdot Q_0 + \text{CLR}' \cdot \text{INC}' \cdot Q_1$$
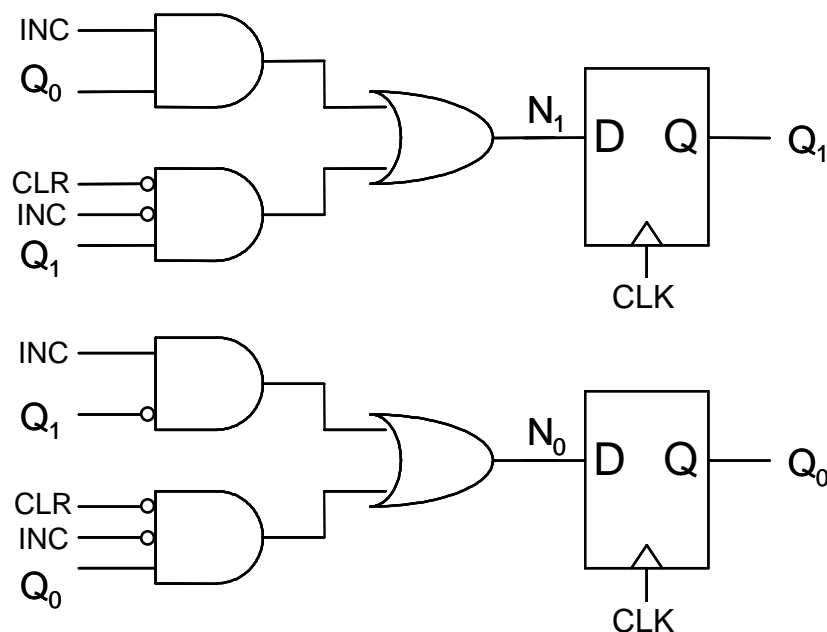
$$N_0 = \text{INC} \cdot Q_1' + \text{CLR}' \cdot \text{INC}' \cdot Q_0$$



- 14.2 Modify the transition table for the counter in the previous problem to contain a static output. This output (call it Z) should be asserted any time the current counter value is not equal to '00'. Finally, write the equation for Z.

CLR	INC	Q <sub>1</sub>	Q <sub>0</sub>	N <sub>1</sub>	N <sub>0</sub>	Z
0	0	0	0	0	0	0
0	0	0	1	0	1	1
0	0	1	0	1	0	1
0	0	1	1	1	1	1
0	1	0	0	0	1	0
0	1	0	1	1	1	1
0	1	1	0	0	0	1
0	1	1	1	1	0	1
1	0	0	0	0	0	0
1	0	0	1	0	0	1
1	0	1	0	0	0	1
1	0	1	1	0	0	1
1	1	0	0	0	1	0
1	1	0	1	1	1	1
1	1	1	0	0	0	1
1	1	1	1	1	0	1

		CLR INC			
Q <sub>1</sub> Q <sub>0</sub>	Z	00	01	11	10
		0	0	0	0
00		0	0	0	0
01		1	1	1	1
11		1	1	1	1
10		1	1	1	1

$$Z = Q_0 + Q_1$$

- 14.4 Design a 2-bit up/down counter. When CLR = '1' it should clear. Otherwise, the UP/DOWN# signal is as follows: '0' = decrement, '1' = increment.

For simplicity, we will refer to UP/DOWN# as simply U in this solution.


CLR	U	Q <sub>1</sub>	Q <sub>0</sub>	N <sub>1</sub>	N <sub>0</sub>
0	0	0	0	1	1
0	0	0	1	0	0
0	0	1	0	0	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	-	-	-	0	0

		CLR U			
Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
		00	01	11	10
N <sub>1</sub>	00	1			
	01		1		
	11	1			
	10		1		

		CLR U			
Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
		00	01	11	10
N <sub>0</sub>	00	1	1		
	01				
	11				
	10	1	1		

$$N_1 = \text{CLR}' \cdot U' \cdot (Q_1' \cdot Q_0' + Q_1 \cdot Q_0) + \text{CLR}' \cdot U \cdot (Q_1' \cdot Q_0 + Q_1 \cdot Q_0')$$


$$N_0 = \text{CLR}' \cdot Q_0'$$

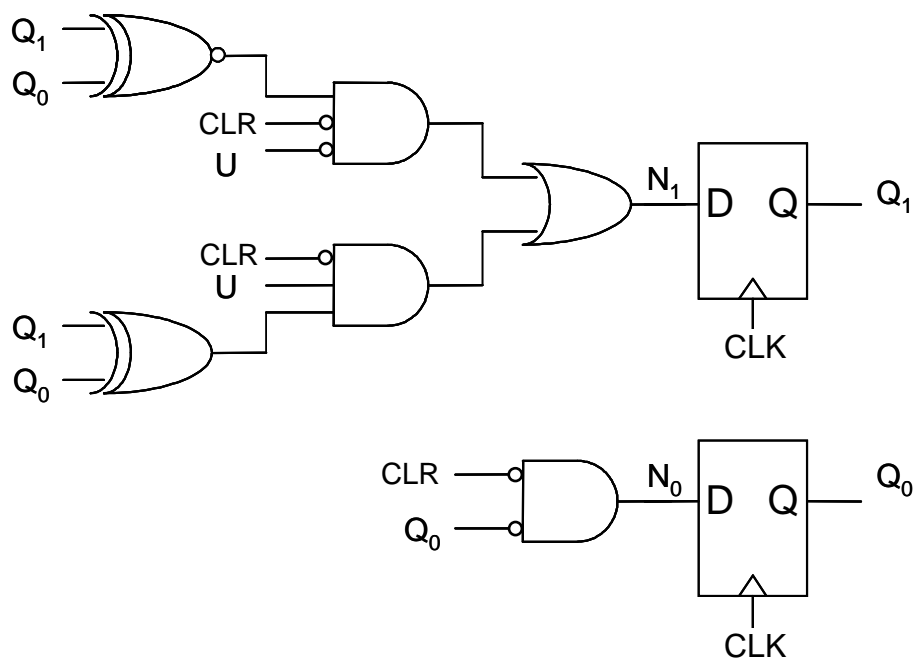

- 14.5 Below is a timing diagram for the counter of Figure 14.6. Complete the waveforms for Z and Y assuming the counter value starts as '00'. Use approximate timing.

INC	Q1	Q0	N1	N0	Z	Y
0	0	0	0	0	0	0
0	0	1	0	1	0	0
0	1	0	1	0	0	0
0	1	1	1	1	1	0
1	0	0	0	1	0	0
1	0	1	1	0	0	0
1	1	0	1	1	0	0
1	1	1	0	0	1	1

Figure 14.6

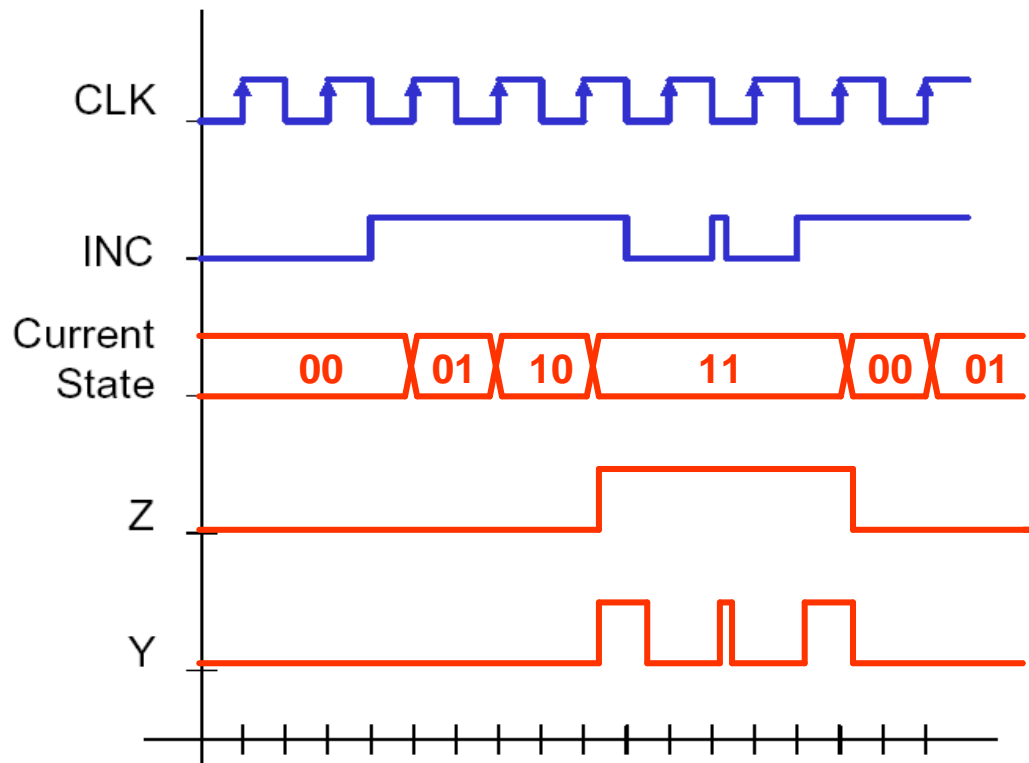

- 14.6 Determine what happens when  $INC = CLR = '1'$  in the case of the transition table shown in Figure 14.5.

CLR	INC	Q1	Q0	N1	N0
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	1	1
0	1	1	1	0	0
1	0	0	0	0	0
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	0	0
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

Figure 14.5

		CLR INC			
Q <sub>1</sub> Q <sub>0</sub>		00	01	11	10
N <sub>1</sub>	00			x	
	01		1	x	
	11	1		x	
	10	1	1	x	

		CLR INC			
		00	01	11	10
Q <sub>1</sub> Q <sub>0</sub>	00		1	x	
	01	1		x	
	11	1		x	
	10		1	x	

$$N_1 = INC \cdot Q_1' \cdot Q_0 + CLR' \cdot INC' \cdot Q_1 + CLR' \cdot Q_1 \cdot Q_0'$$

$$N_0 = CLR' \cdot INC' \cdot Q_0 + INC \cdot Q_0'$$

For  $INC = CLR = '1'$ , these equations become:

$$N_1 = Q_1' \cdot Q_0$$

$$N_0 = Q_0'$$

Thus we have the transition table rows shown below. Notice that the first two and the last row have the behavior of incrementing, whereas the third row has the behavior or decrementing.

CLR	INC	Q1	Q0	N1	N0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	0	1
1	1	1	1	0	0