

ECEn/CS 224

Chapter 11 Homework Solutions

- 11.1 Below is a timing diagram for the SR latch of Figure 11.1. Fill in the output waveform. Reflect approximate timing. See section 11.7 to remind you what is meant by *approximate timing*.



 



Figure 11.1: SR Latch

 

 
- 11.2 Repeat Problem 11.1 but with detailed timing. You may simply label each output signal transition in the timing diagram with the time it occurs. Delays of the various gates include: $t_{NOT} = 1ns$, $t_{AND} = 3ns$, $t_{NOR} = 2ns$.



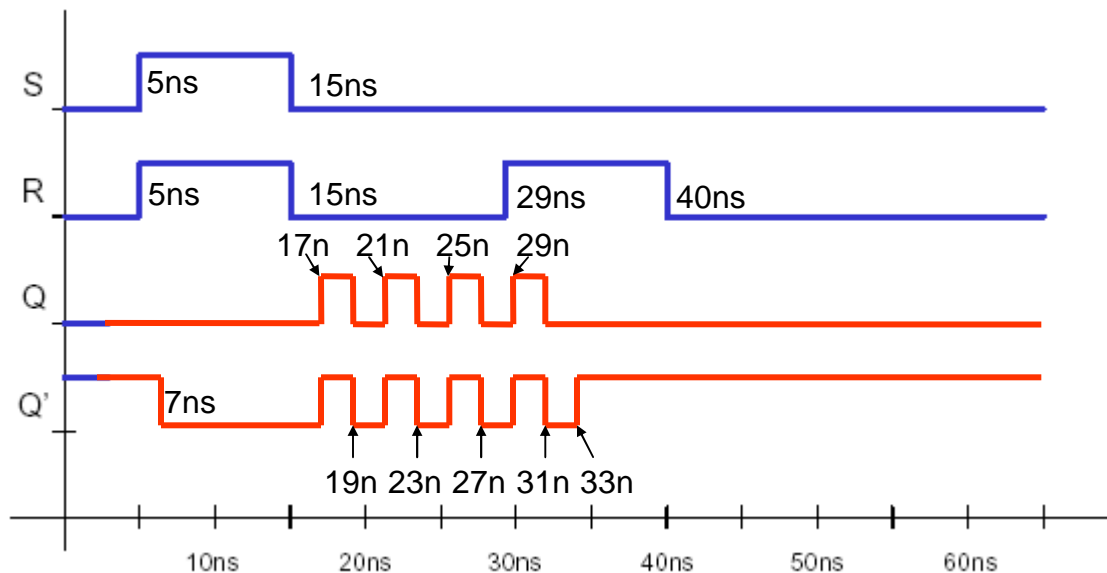- 11.3 Complete the timing diagram below for an SR latch. In this case, the circuit oscillates. Use $t_{NOR} = 2ns$ and accurately reflect the Q and Q' waveforms in the drawing (complete with timing).



 - 11.5 Shown in the figure below is a storage circuit made from NAND gates instead of NOR gates. Experiment with values on the S and R inputs to determine how it works. Hint: start with $S=R=1$. Write a transition table to summarize what you find.



Notice the similarity to the NOR latch.

- 11.6 Below is a timing diagram for the circuit of Figure 11.7. Fill in the output waveform. Reflect approximate timing.



 


Figure 11.7: Gated D Latch

 

 - 11.7 Repeat Problem 11.6 but with detailed timing. Use the following delays: $t_{NOT} = 1ns$, $t_{AND} = 3ns$, $t_{NOR} = 2ns$.



- 11.11 Below is a timing diagram for the circuit of Figure 11.18. Fill in the output waveform. Reflect approximate timing.


 


Figure 11.18 Rising Edge Triggered Master/Slave D Flip Flop

 


22ns

82ns

22ns

82ns


 
- 11.12 Repeat Problem 11.11 but with detailed timing. For your delays use the following:
 $t_{CLK-Q} = 2ns$, $t_{setup} = 4ns$, $t_{hold} = 3ns$. Which of these delays is actually needed in order to complete the timing diagram?



When only t_{CLK-Q} is given, it should be treated as a worst case delay from the clock edge to either Q or Q'. Therefore, in the timing diagram, there isn't a difference between when Q changes and Q' changes.

For this example, only t_{CLK-Q} is required to complete the timing diagram.

  - 11.14 Below is a toggle circuit along with a timing diagram. Complete the associated timing diagram complete with detailed timing. Use the delays from Problem 11.12. Also, use $t_{\text{NOT}} = 2\text{ns}$.



11.17 Discuss the problems associated with using flip flops with asynchronous clear or preset signals. In particular, address the following: (a) false outputs on the logic generating the asynchronous control signals and (b) timing issues associated with the asynchronous control signals.

- a) Because asynchronous signals are constantly monitored by the flip-flop, any false output or glitch may cause the flip flop to be cleared or set. Because of this, the logic generating these asynchronous signals must be hazard free.
- b) First, there will be a minimum pulse width on the asynchronous signals similar to t_{setup} . This minimum is required to ensure that the flip flop is completely set or cleared by the input. Otherwise, correct clear/preset behavior may not be guaranteed.

Second, an asynchronous input to a flip flop must not be released too close to the asserting clock edge (i.e., it should not be released during the t_{setup} period). Otherwise some of the flip flops may take on their cleared/preset values and others may take on the value on their inputs. These asynchronous signals should only be released after the clock edge and before the next t_{setup} period to ensure that all of the flip flops in the circuit come out of reset correctly in the same clock cycle.