

ECEn/CS 224

Cascaded Counter Homework Solutions

- Create a 6-bit binary counter from two 3-bit counter modules. Assume that the 3-bit counter has the following inputs and outputs: **enable** (when enable=1 the counter increments, when enable = 0, the counter keeps its original value), **clr** (when clr = 1, the counter will reset to "000" on the next clock edge), **clk** (a positive edge triggered clock), and **out[2:0]** (the 3-bit output of the counter). Note that you will have to create your own "rollover" signal for the first 3-bit counter module. For this problem, draw a schematic of your counter and create a timing diagram of your counter that demonstrates the counter sequencing from the value "000000" to "001011".

