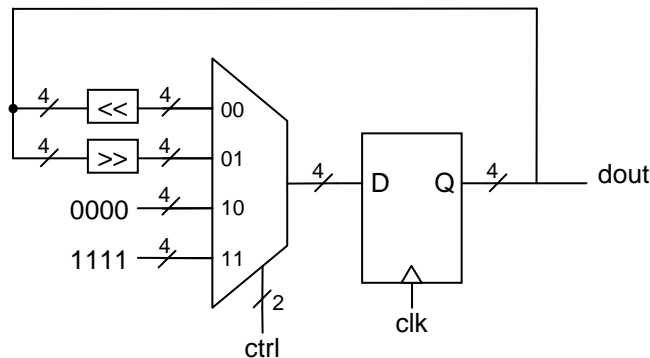


ECEn/CS 224


Chapter 12 Homework Solutions

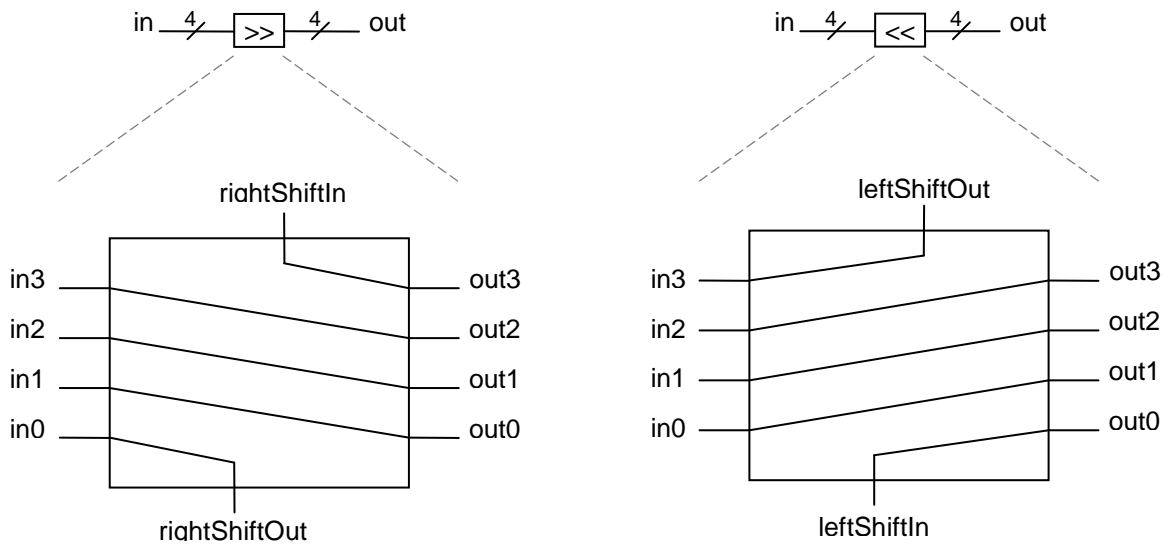- 12.1 Design a 4-bit shift register with the following functionality: shift-left, shift-right, clear, load-all-1's. Use a 2-bit control input to select between these options (00=shift-left, 01=shift-right, 10=clear, 11=load-all-1's).

A schematic drawing of the circuit is shown below.




The 1-bit shifters are implemented simply by changing the way the output of the flip flop is connected to the input of the mux, as shown below. Optional shiftIn inputs and shiftOut outputs are also shown. For this problem, it's alright to assume that the value 0 is shifted in and the value that is shifted out is ignored.



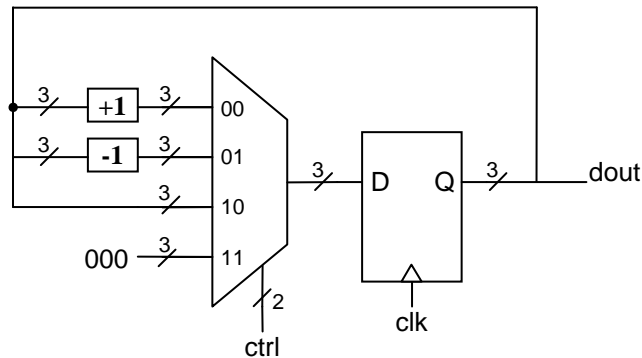
- 12.2 Design a 3-bit up/down counter with the following functions: increment, decrement, no change, reset. Use a 2-bit control input to select between these options (00=increment, 01=decrement, 10=no change, 11=reset). You may assume you have an already-designed '+1' block available for your use as well as an already-designed '-1' block available for your use.





A schematic drawing of the circuit is shown below.



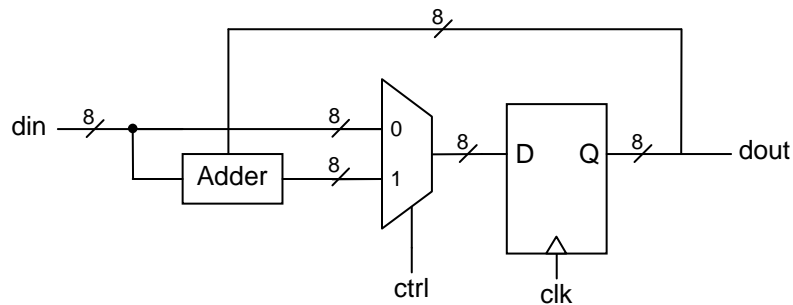- 12.3 Design an accumulator. This is a circuit which takes in an 8-bit value and a single control input. When the control input is '0', the accumulator register loads the 8-bit input value. When the control input is '1', the accumulator adds the 8-bit input value to the value already stored in the accumulator register and makes it the new accumulator register value. Design this all the way down to the level of gates and flip-flops.

The top level schematic is shown below, followed by the individual blocks. The carry out of the adder would normally be ignored.



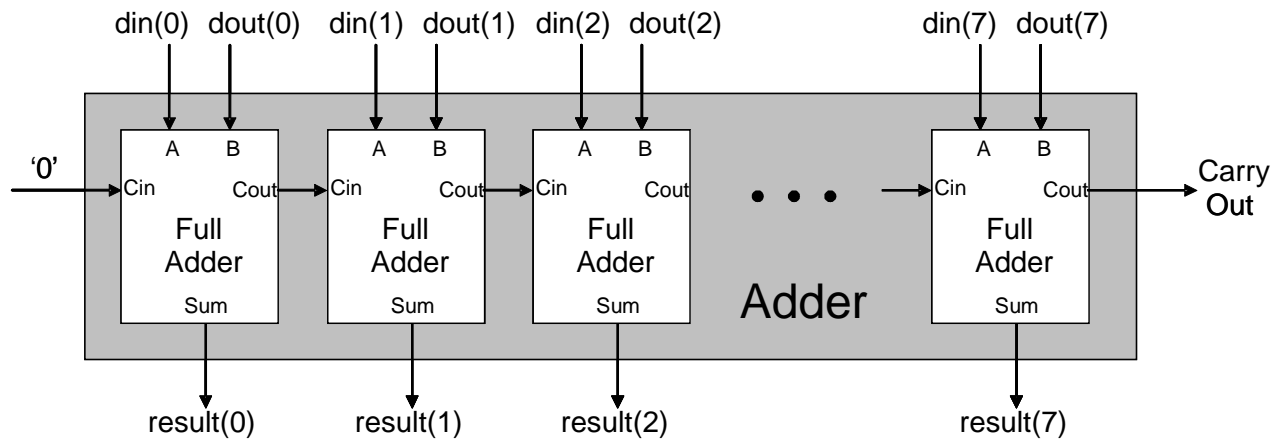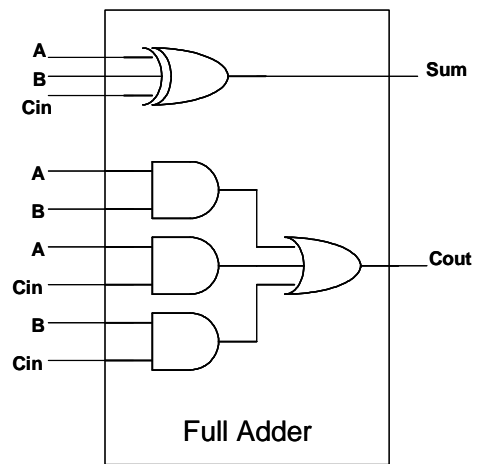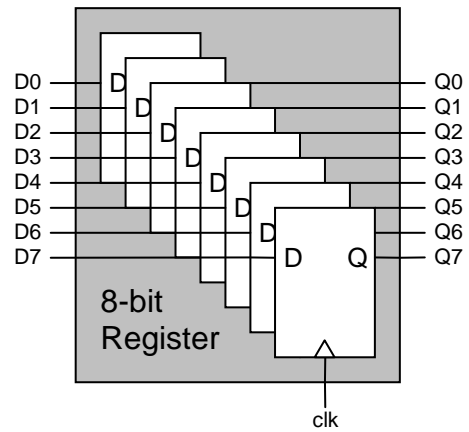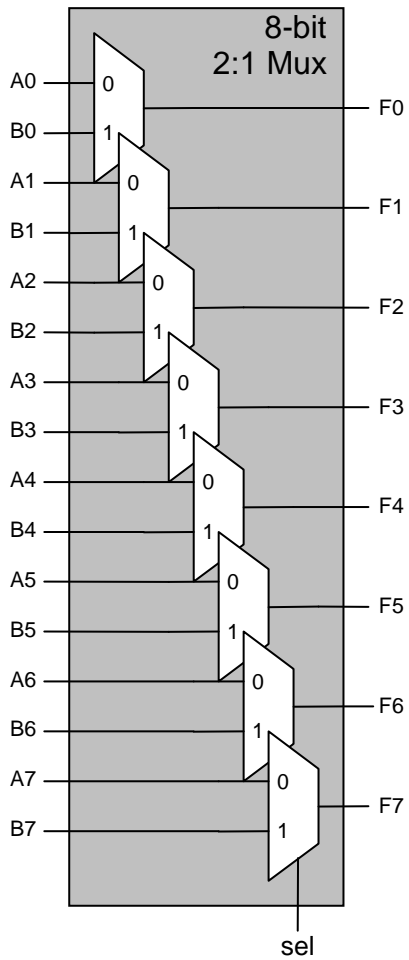

- 12.4 Design a 4-bit ring counter. This is a 4-bit shift register. When the control input is high, the register loads the value '1000', when the control input is low, the count sequence is:

'1000' → '0100' → '0010' → '0001' → '1000' → ...

